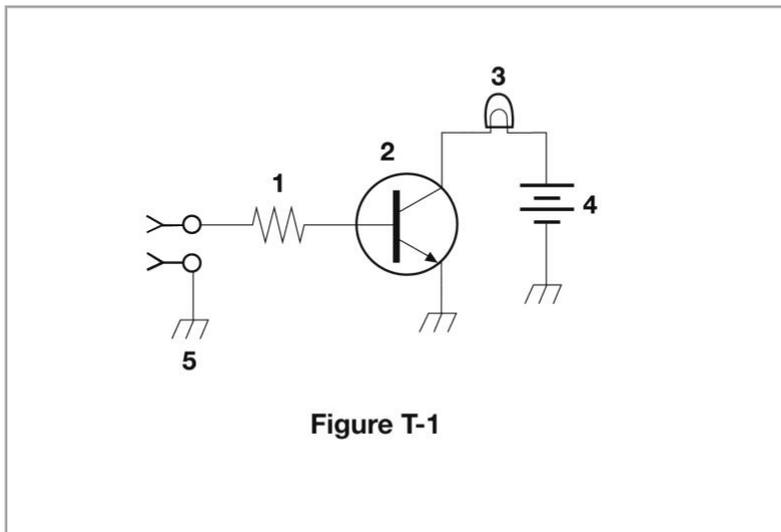


Schematics

Schematic diagrams show how components are interconnected. Below are the three schematics you may see on the exam, with the components identified in a list.



- 1 Resistor
- 2 Transistor
- 3 Lamp
- 4 Battery
- 5 Ground symbol

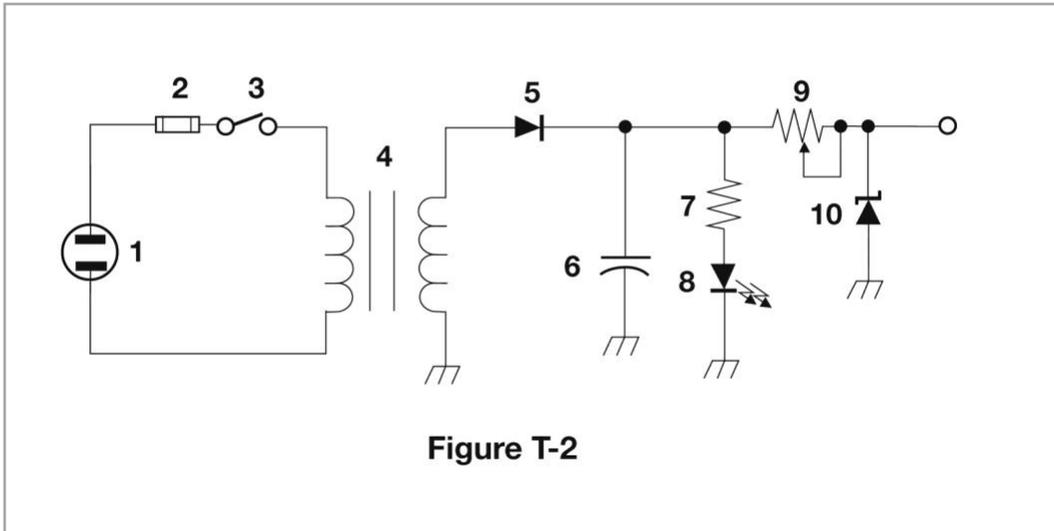


Figure T-2

- 1 AC Plug
- 2 Fuse
- 3 Switch
- 4 Transformer
- 5 Diode
- 6 Capacitor
- 7 Resistor
- 8 Light emitting diode (LED)
- 9 Variable resistor
- 10 Zener diode

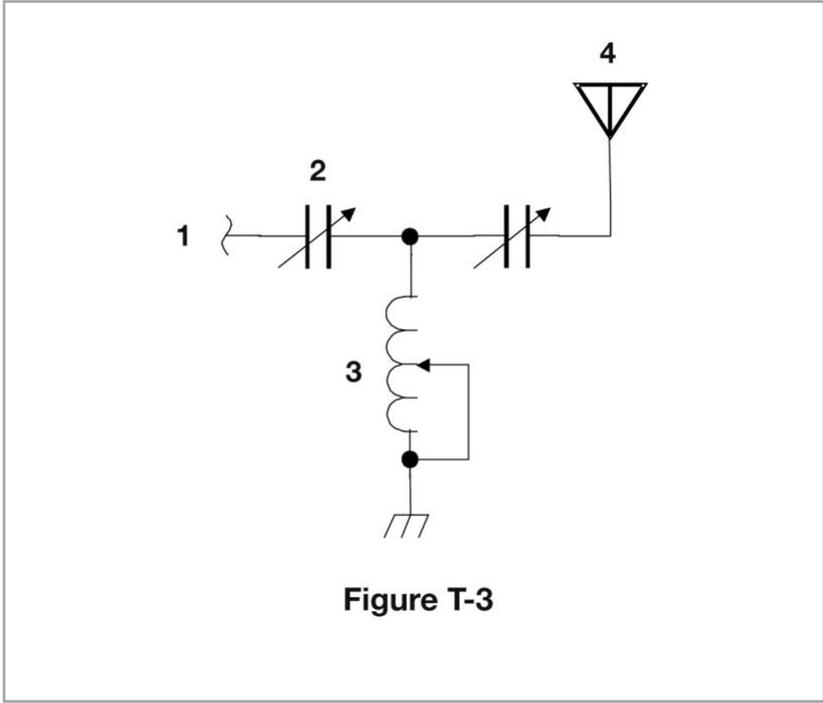


Figure T-3

- 2 Variable capacitor
- 3 Variable inductor
- 4 Antenna